

# Ultra-Wideband Digital Receiver – LNA Design


Won Namgoong

University of Southern California

# Why UWB Digital Receiver?


- Digital receivers perform receiver functions (e.g., correlation) digitally.
- Higher performance.
  - Employ large number of parallel correlators.
    - Need 100+ to exploit available diversity.
    - Not practical in analog receivers.
  - Employ sophisticated interference suppression algorithms.
- Higher levels of integration and lower power.
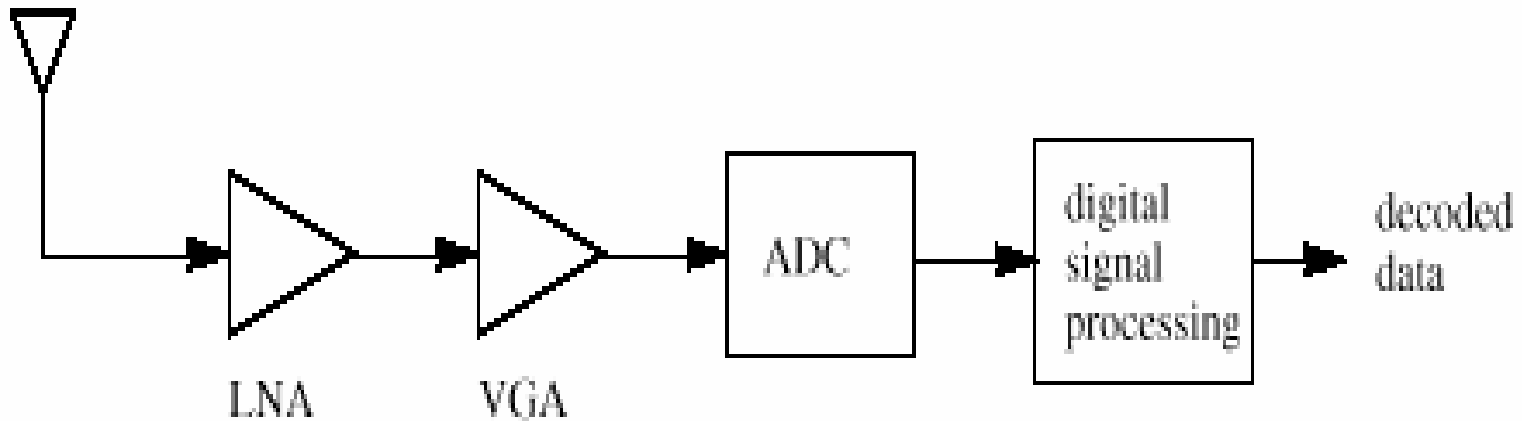
# Basic UWB Digital Receiver Architecture



- Main challenges:
  - Low-noise amplification
  - Data conversion
  - Synchronization

# UWB LNA Design Objectives

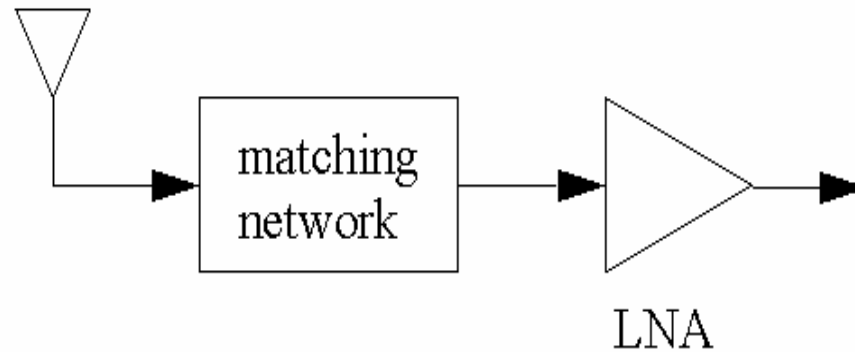


- Minimize noise figure.
  - $NF = (\text{Input SNR})/(\text{Output SNR})$
- Maximize signal voltage gain transfer.
- Minimize power dissipation.

# Existing Work


- Narrowband matching.
    - Single-tone assumption.
      - $NF = (\text{output noise})/(\text{input noise})$
  - Broadband matching (1970's).
    - Average single-tone noise figure.
      - No signal information.
- Develop matching technique that maximizes output SNR.

# SNR Definition

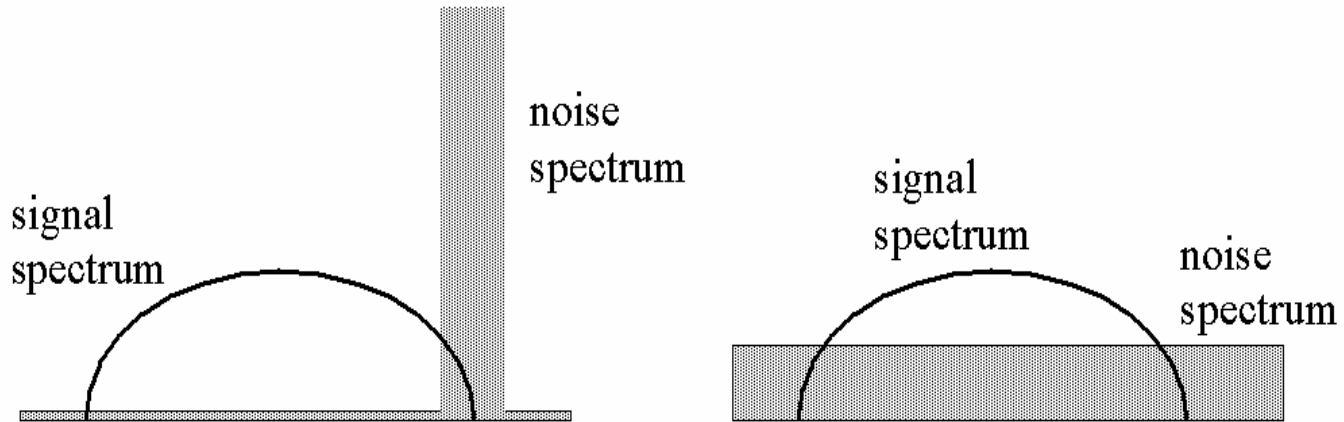


- SNR should depend on signal and noise spectrum.
- SNR defined as the matched filter bound.
  - Whitened matched filter for one-shot transmission.
  - Maximum achievable performance in a data transmission system.

# Problem Formulation

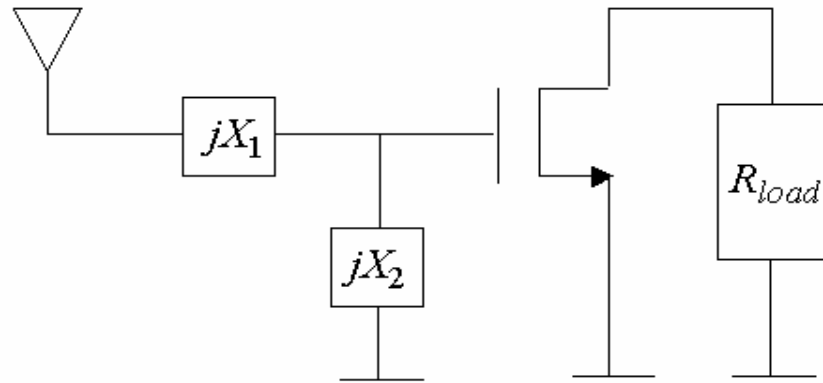


- Maximize output SNR for a given voltage gain while minimizing power dissipation.
- Matching circuits are lossless.
- Common source amplifier.

# Equivalent Circuit Model

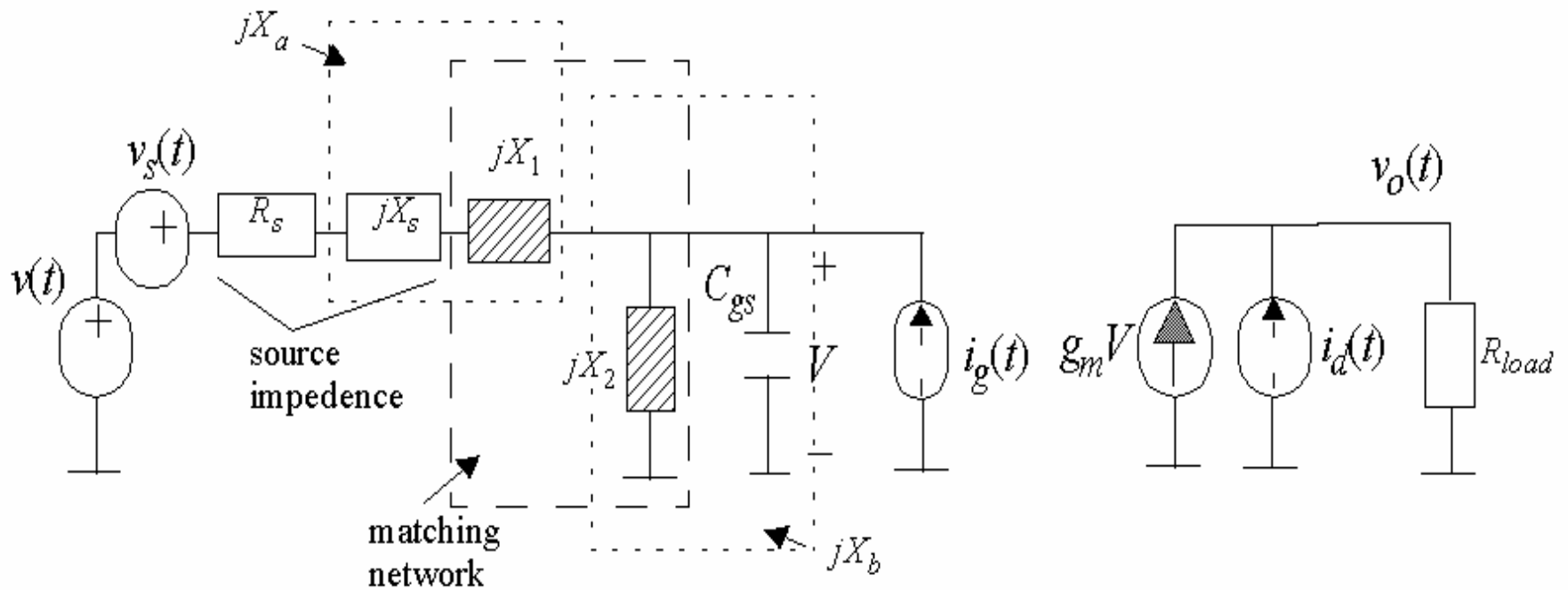



# Equivalent System Model

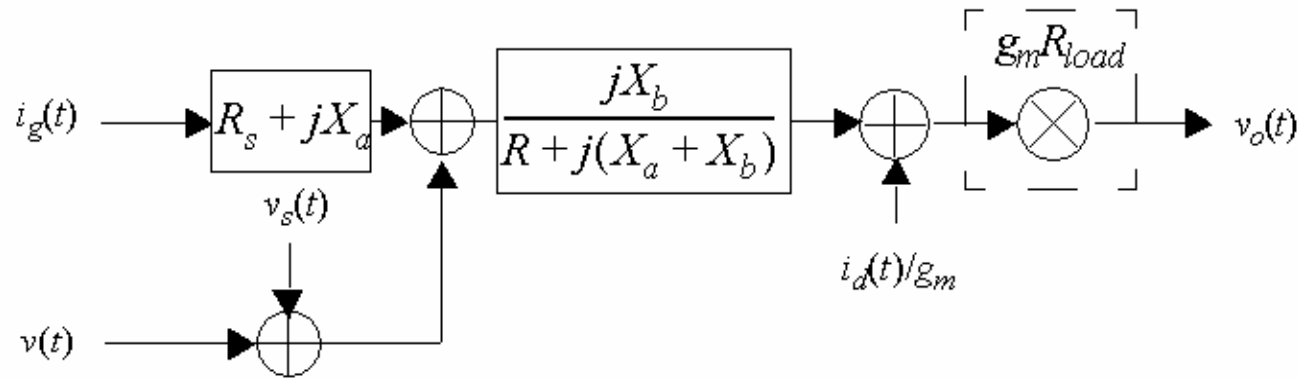

- Design  $X_a(\omega)$  and  $X_b(\omega)$  to maximize output SNR.
  - Maximize signal voltage gain.
  - Minimize gate noise current gain.
  - Cancel gate and drain noise current.

# Optimum LNA Matching


- Differentiate noise figure equation to solve for optimal  $X_a(\omega)$  and  $X_b(\omega)$ .
- Resulting minimum noise figure given by

$$NF_{min} = \frac{\int |P(\omega)|^2 d\omega}{\int \frac{|P(\omega)|^2}{1 + \frac{\omega}{\omega_T} \sqrt{\frac{\delta\gamma}{5}} (1 - |c|^2)} d\omega}$$

# Suboptimal LNA Matching


- Choose circuit structure that best approximates optimal  $X_a(\omega)$  and  $X_b(\omega)$ .
- Perform numerical gradient search (e.g., Gauss-Newton method) to solve for L's and C's that minimize noise figure.
  - Initial point based on optimum  $X_a(\omega)$  and  $X_b(\omega)$ .

# Example

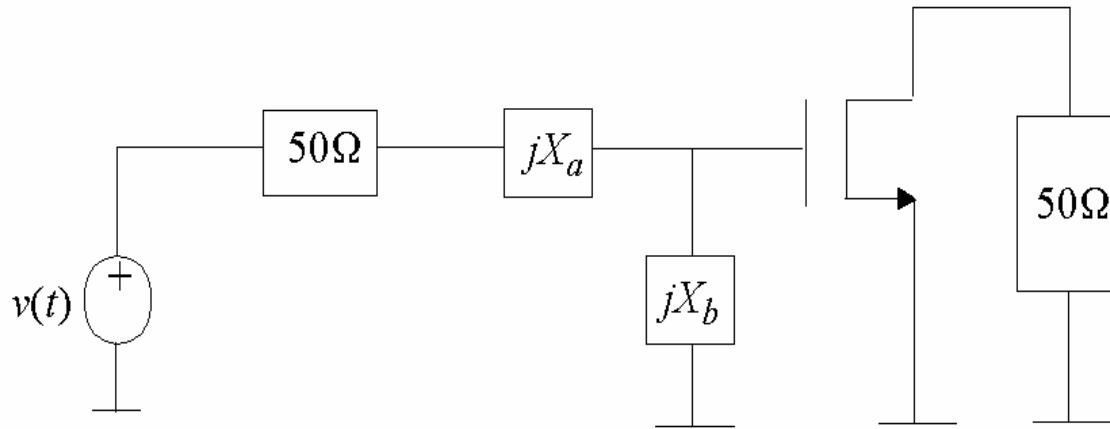


- Assume source and load impedance are  $50\ \Omega$ .
- Received signal is 2<sup>nd</sup> derivative of Gaussian pulse.
- Standard  $0.35\mu\text{m}$  CMOS process.

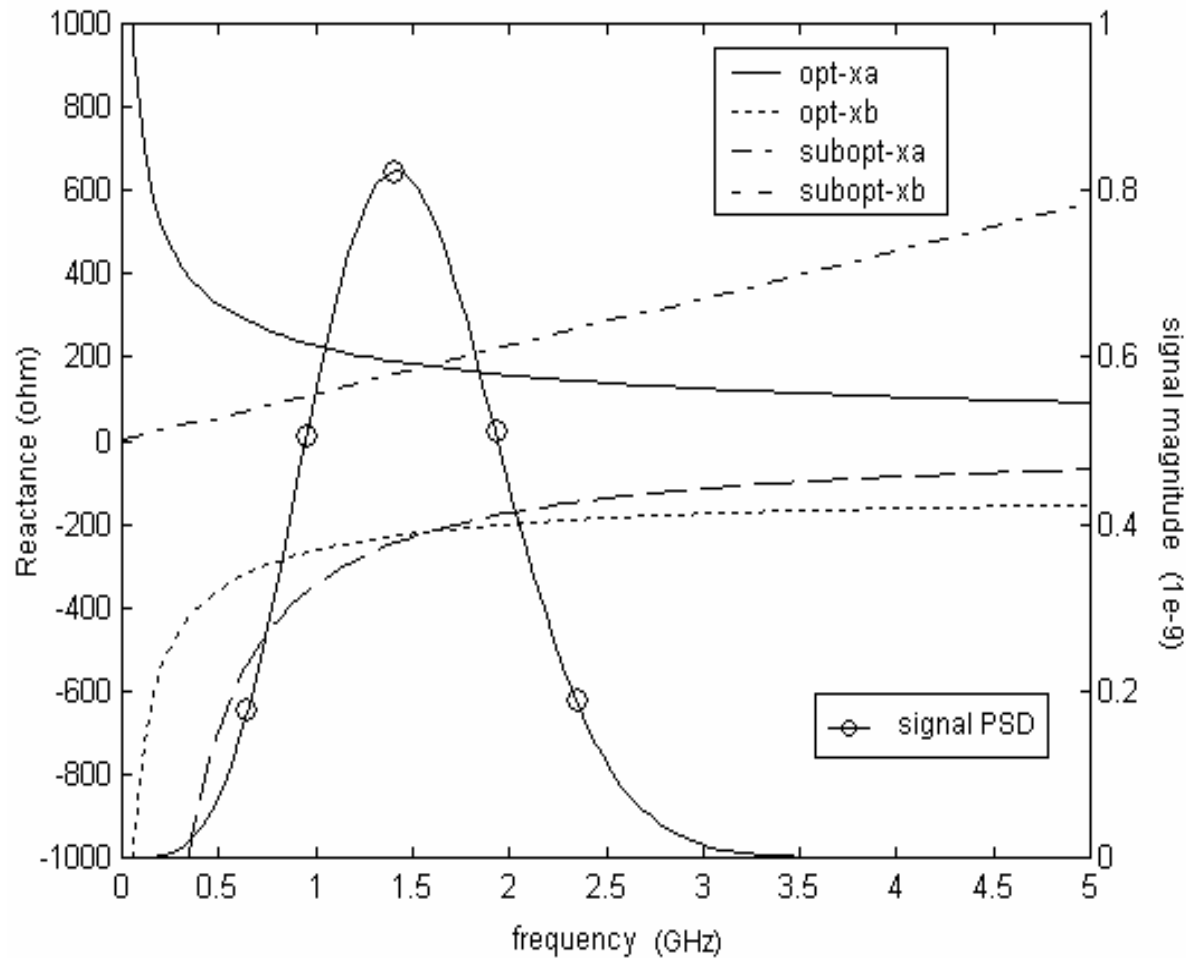
# Design of $X_a(\omega)$ and $X_b(\omega)$




# Voltage Gain in Matching Network

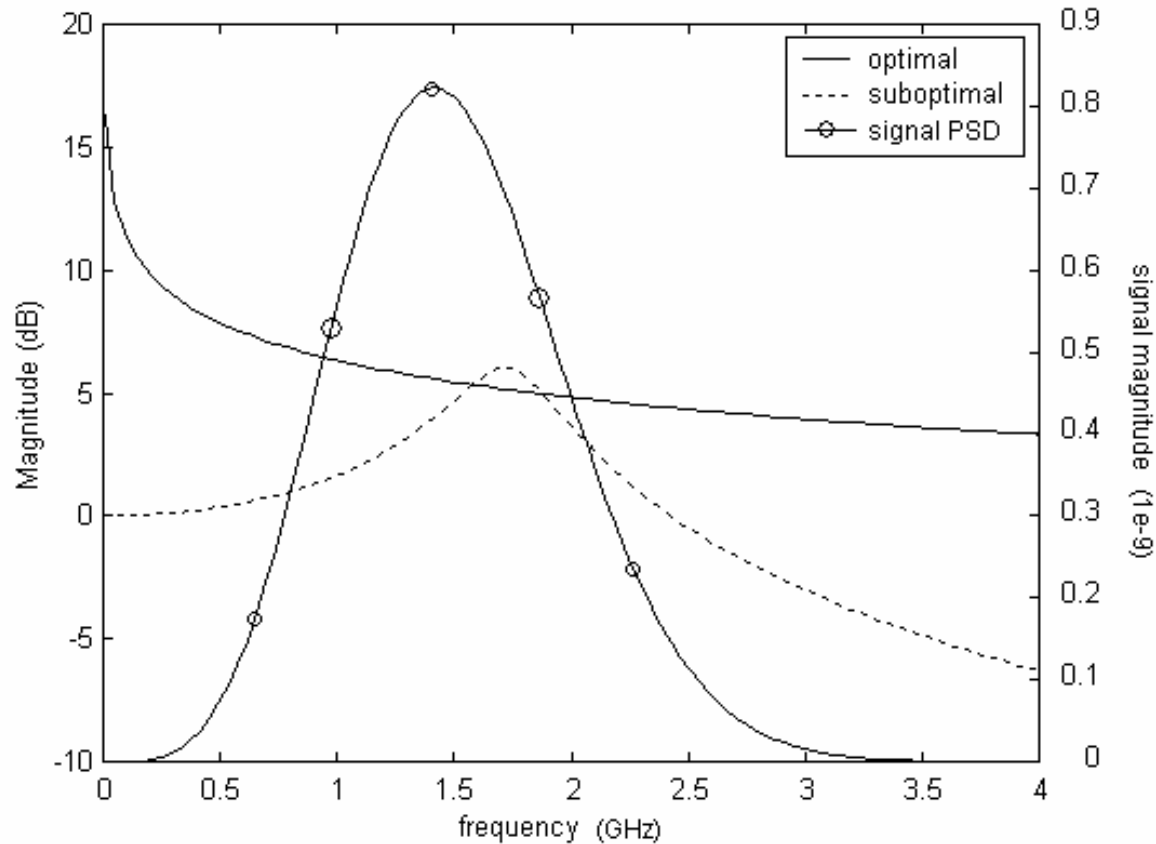

# Noise Figure vs. Signal Gain

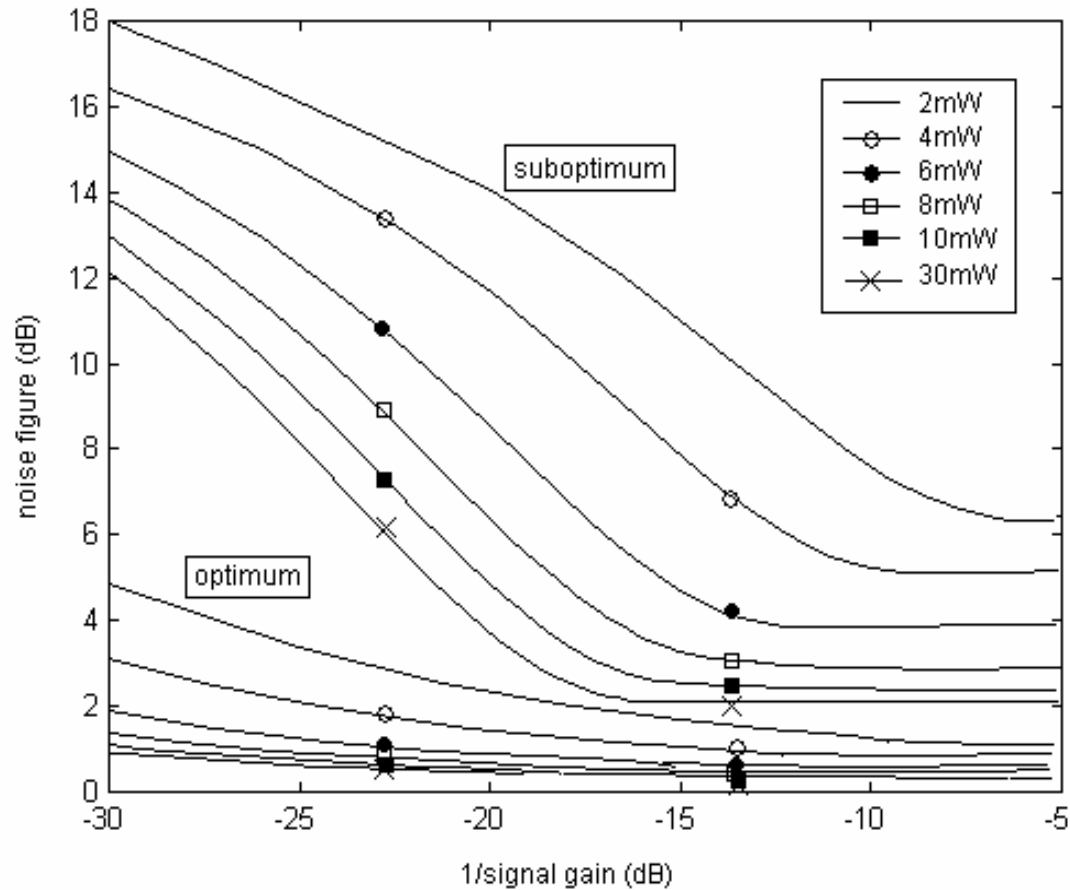

# Effect of Gaussian Pulse Width

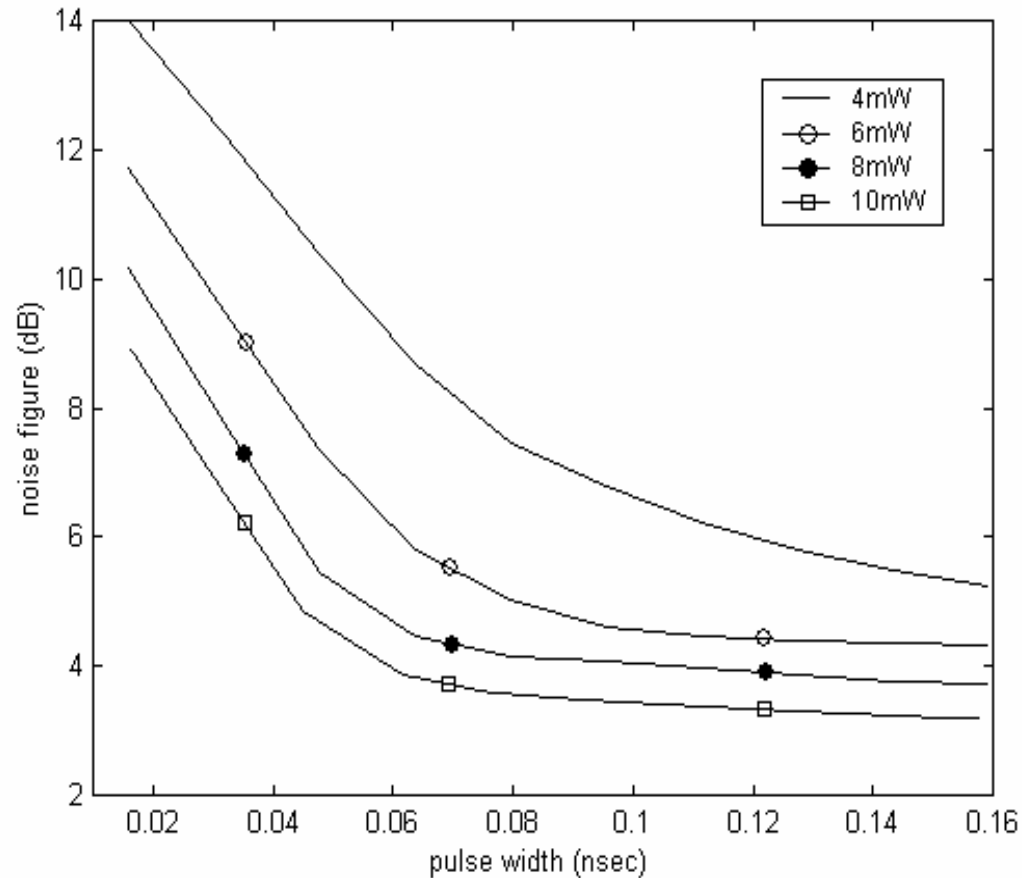



# Conclusion

- Developed LNA design methodology suitable for wideband systems.
  - Maximizes output SNR, which is defined as the matched filter bound.
  - Applies equally to broadband and narrowband systems.
- Need multiple stages for efficient amplification.
- Large LNA power dissipation for very narrow transmit pulse ( $< 0.1\text{nsec}$ ).
- Implement UWB receiver prototypes.